

CSE 577 Spring 2011

Operational Amplifier Design

Insoo Kim, Jaehyun Lim, Kyungtae Kang, Kyusun Choi


Mixed Signal CHIP Design Lab.

Department of Computer Science & Engineering

The Pennsylvania State University


2 Stage OP Amp Design

2 Stage OP Amp

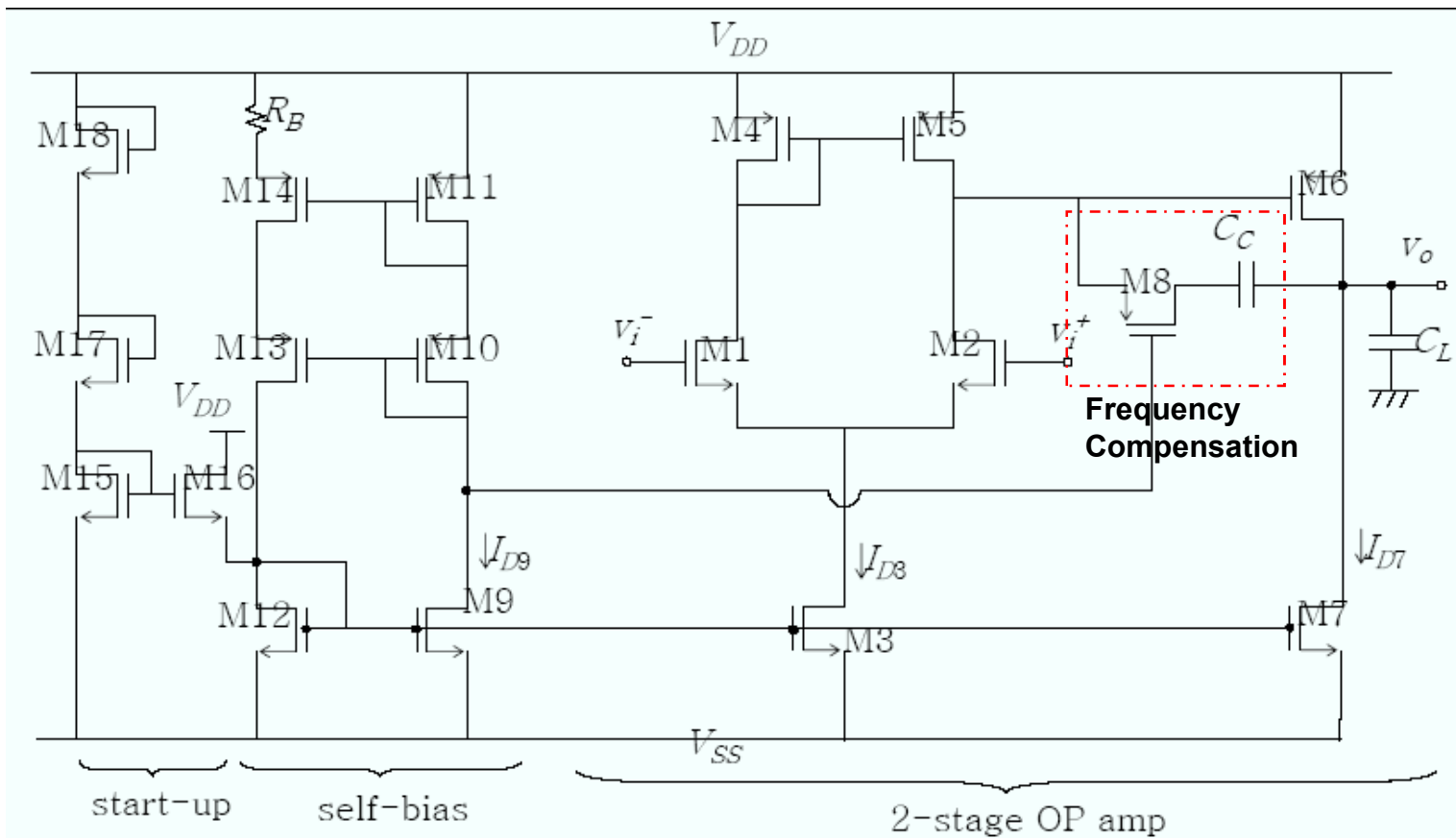

[Reminder] Common Mode

■ Common Mode Gain

 

$$\frac{V_{od}}{V_{ic}} = A_{cd} = \frac{g_{m1} - g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D$$

■ Common Mode Rejection Ratio

$$CMRR = \frac{A_{dm}}{A_{cd}} \quad CMRR = (2g_{m1}r_{o5}) \cdot g_{m3}(r_{o1} \parallel r_{o3})$$

■ Common Mode Input Voltage Range

$$V_{SS} + V_{TN1} + V_{DSAT5} + V_{DSAT1} < V_{IC} < V_{DD} - |V_{DSAT3}| - |V_{TP3}| + |V_{TN1}|$$

2 Stage OP Amp Design

■ Design Process

- Model Parameter Extraction (1/6)
 - k_n : 55.84 $\mu\text{A}/\text{V}^2$
 - λ_n : 0.025
 - V_{thn} : 0.776 V
 - k_p : 23.51 $\mu\text{A}/\text{V}^2$
 - λ_p : 0.055
 - V_{thp} : 0.858 V
- Assign Current from Power Consumption Spec. (2/6)
 - Power Consumption : 2 mW
 - Total Current : 0.4 mA @ 5V VDD
 - Input Pair : 0.2 mA
 - Second Stage : 0.2 mA

2 Stage OP Amp Design

■ Design Process

- Determine minimum channel length (3/6)
- Determine channel width (4/6)

- Determine $W_{1,2}$ from voltage gain spec.

$$\begin{aligned} A_v &= g_{m1,2} \cdot (r_{o2} \parallel r_{o4}) \\ &= \sqrt{2\beta \frac{W}{L} I_D} \cdot (r_{o2} \parallel r_{o4}) \end{aligned}$$

- Determine W_5 & Bias Voltage from power consumption & CM min.


$$V_{SS} + V_{TN1} + V_{DSAT5} + V_{DSAT1} < V_{IC}$$

- Determine $W_{3,4}$ from CM max.

$$V_{IC} < V_{DD} - |V_{DSAT3}| - |V_{TP3}| + |V_{TN1}|$$


- Determine Bias Level of Current Source Tr. (5/6)
 - Considering CM min value and the transistor size
- Check other specifications (6/6)
 - Repeat step 4 to 6

A Calculation Example

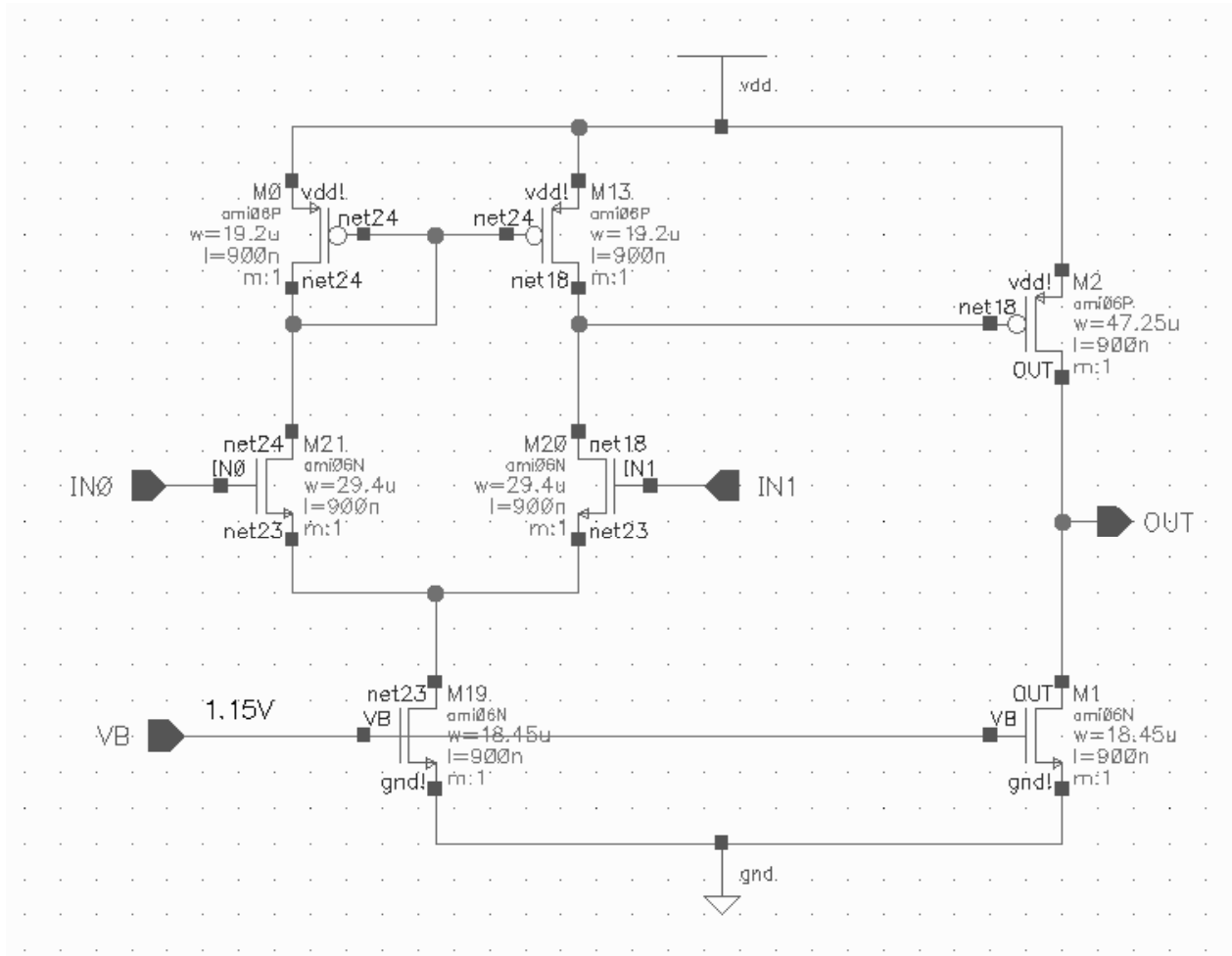

Calculated Gain= 3000 (70dB)


Simulation Results

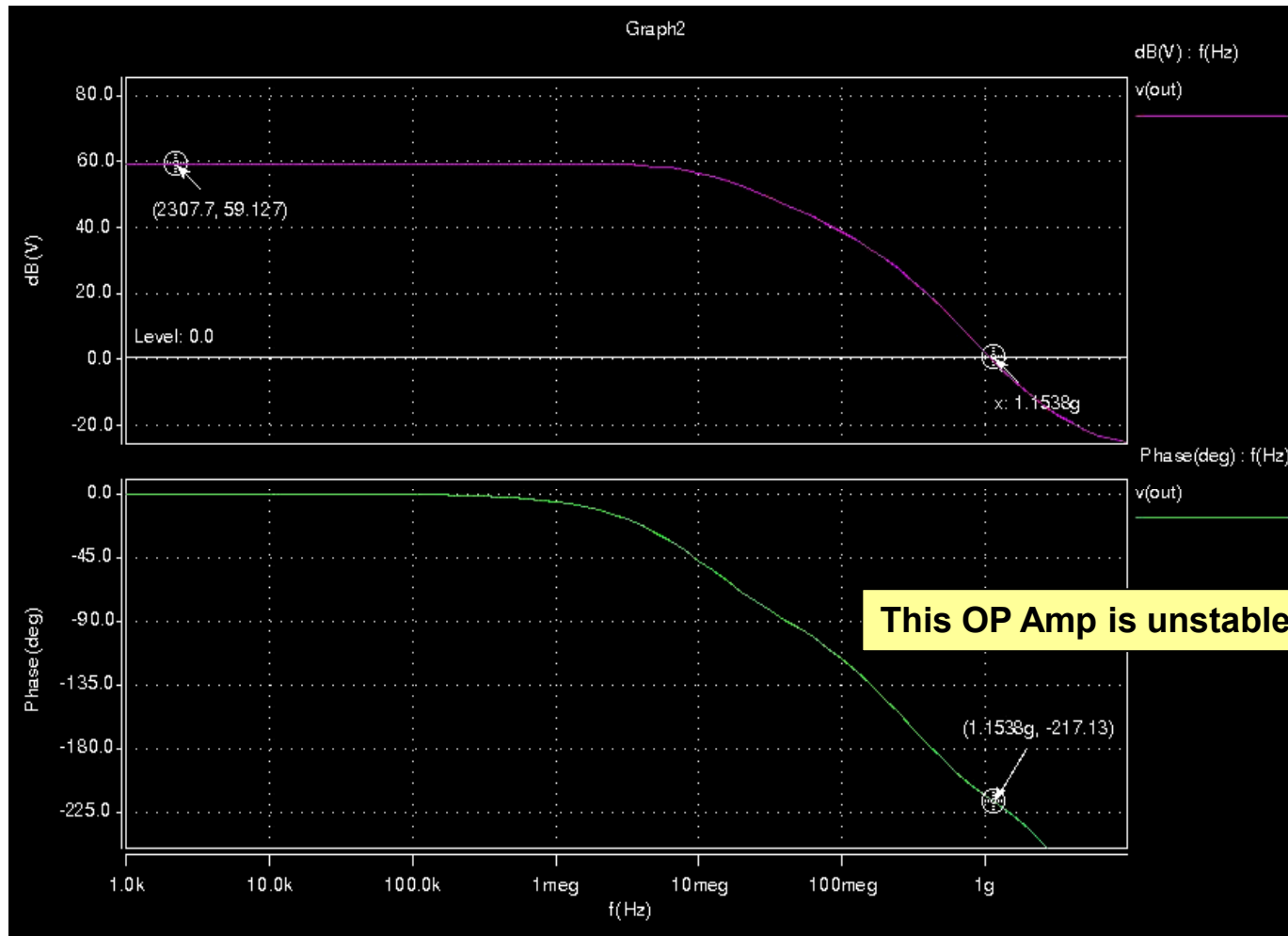

Gain: **59dB**


BW: 1.15 GHz

[Reminder] Feedback & Stability

 

$$A(s) \equiv \frac{V_{out}(s)}{V_{in}(s)} = \frac{A_v(s)}{1 + F \cdot A_v(s)}$$


 
✓ Unstable Condition : $F \cdot A_v(s) = -1$




$$|A_v(s)| = \frac{1}{F} \quad \& \quad \angle A_v(s) = -180^\circ$$

Before Frequency Compensation

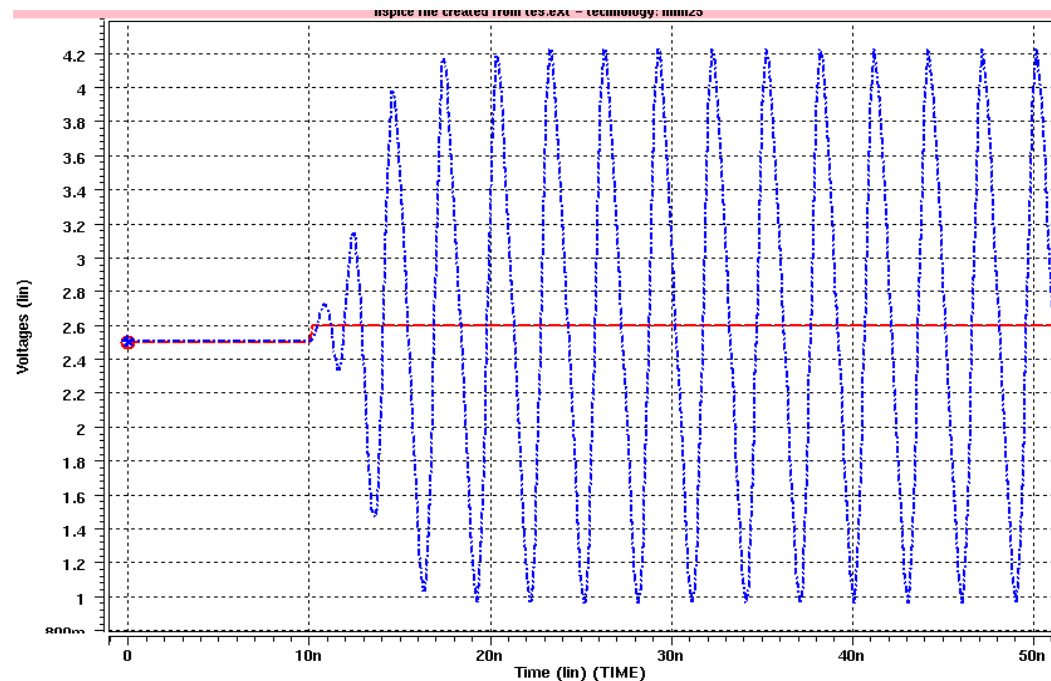 - A unit gain buffer characteristic without frequency compensation



Frequency Analysis

 

KCL at v_6 and v_o nodes

$$G_{m1} \cdot (v_{i2} - v_{i1}) + \left\{ s(C_1 + C_C) + \frac{1}{R_{o1}} \right\} \cdot v_6 - sC_C \cdot v_o = 0$$

$$(G_{m2} - sC_C) \cdot v_6 + \left\{ s(C_L + C_C) + \frac{1}{R_{o2}} \right\} \cdot v_o = 0$$

(cont'd) Frequency Analysis

$$A_{dv}(s) = \frac{v_o}{v_{i2} - v_{i1}} = \frac{(G_{m1}R_{o1}) \cdot (G_{m2}R_{o2}) \cdot (1 - sC_C/G_{m2})}{\left[1 + s \cdot \{C_L R_{o2} + C_1 R_{o1} + C_C \cdot (G_{m2}R_{o2}R_{o1} + R_{o1} + R_{o2})\} \right. \\ \left. + s^2 \cdot \{C_1 C_L + (C_1 + C_L) C_C\} \cdot R_{o1} R_{o2} \right]}$$

$$A_{dv}(s) = \frac{A_{dv}(0) \cdot \left(1 - \frac{s}{z_1}\right)}{\left(1 - \frac{s}{p_1}\right) \cdot \left(1 - \frac{s}{p_2}\right)} \approx \frac{A_{dv}(0) \cdot \left(1 - \frac{s}{z_1}\right)}{1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}}$$


Dominant pole approximation: $|p_1| \ll |p_2|$

$$p_1 = \frac{-1}{C_C \cdot (G_{m2}R_{o2}R_{o1} + R_{o1} + R_{o2}) + C_L R_{o2} + C_1 R_{o1}} \approx \frac{-1}{R_{o1} \cdot G_{m2}R_{o2} \cdot C_C}$$

$$p_2 = \frac{+1}{p_1 \cdot \{C_C(C_1 + C_L) + C_1 C_L\} R_{o1} R_{o2}} = \frac{-G_{m2}C_C}{C_C(C_1 + C_L) + C_1 C_L}$$


Positive Zero & Pole-Zero Cancellation

- Feed Forward

 


Positive Zero & Pole-Zero Cancellation

- Pole-Zero Cancellation

 



$$z_1 = \frac{G_{m2}}{C_C} \cdot \frac{1}{1 - G_{m2} \cdot R_Z}$$

An Example of Frequency Compensation

 

After Frequency Compensation

  - A unit gain buffer characteristic with frequency compensation



Frequency Compensation must be considered in designing OP Amps



Folded Cascode Op Amp

Basic Folded Cascode

Design of Single Ended Folded Cascode

Cascode Stage


■ Small Signal Analysis

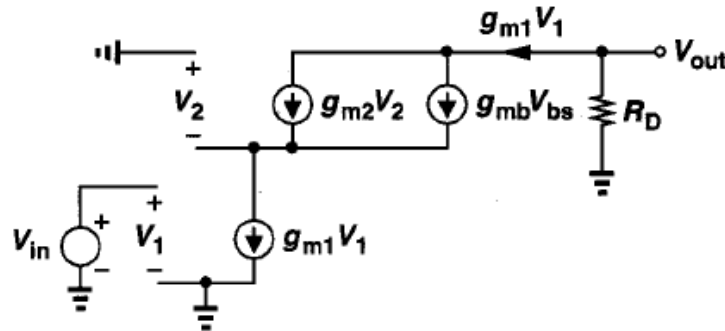 

$$V_{out} = (R_{out} \parallel R_D) \cdot g_{m1} V_{in}$$

$$A_v = g_{m1} \cdot (R_{out} \parallel R_D)$$

■ Rout

 


$$R_{out} = r_{o1} \cdot [(g_{m2} + g_{mb2})r_{o2} + 1] + r_{o2}$$

$$\approx r_{o2} \cdot [r_{o1} \cdot (g_{m2} + g_{mb2}) + 1]$$

Folded Cascode Stage

■ Schematic

 

■ Advantages


- Wider Operating Range than telescopic cascode stage
- Easy to set Common Mode Voltage

■ Disadvantages

- Limited Output swing
- Large Voltage Headroom
- Large Power Consumption


Single Ended Folded Cascode Op Amp

■ Circuit Configuration

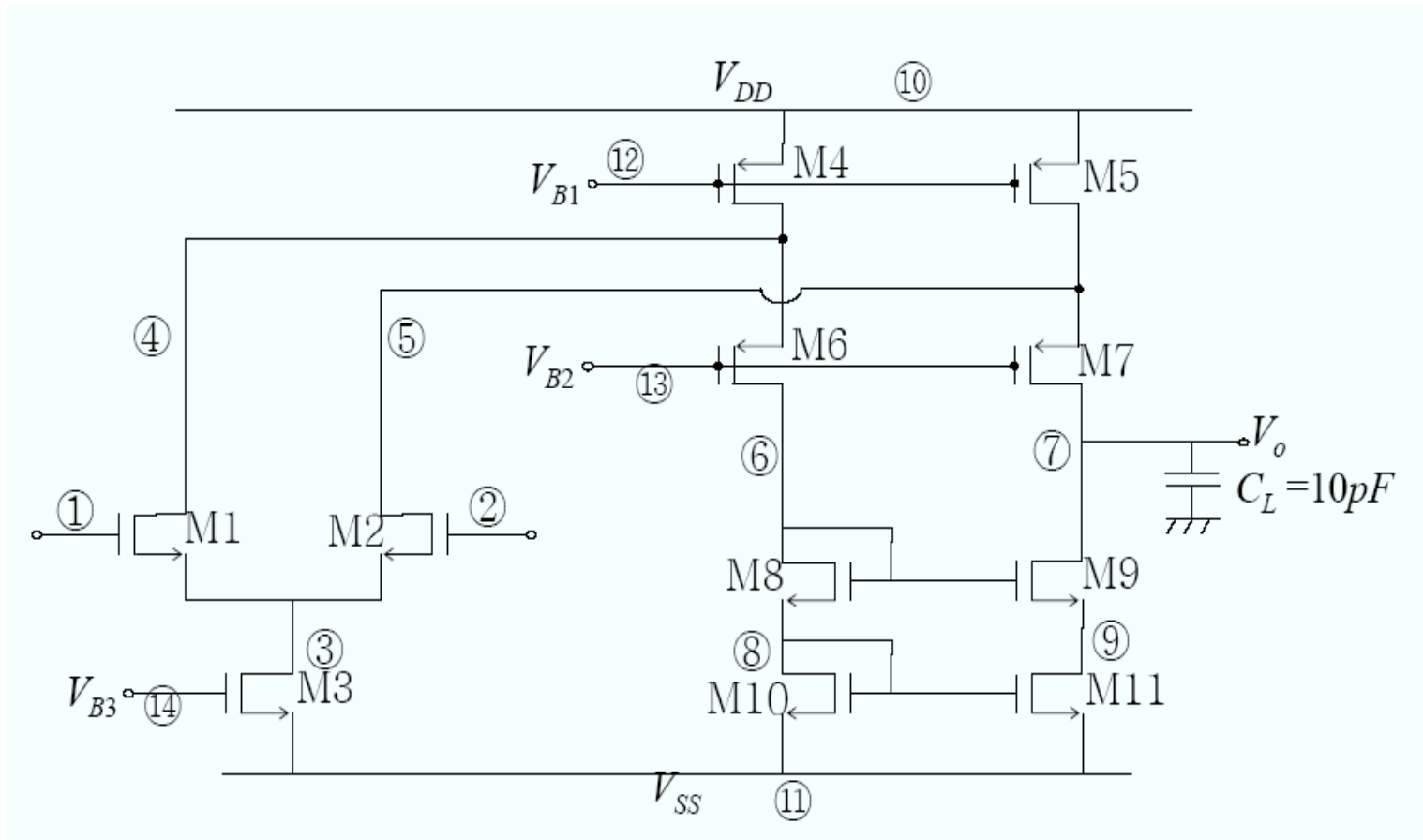

(cont'd) Single Ended Folded Cascode Op Amp

■ Gm

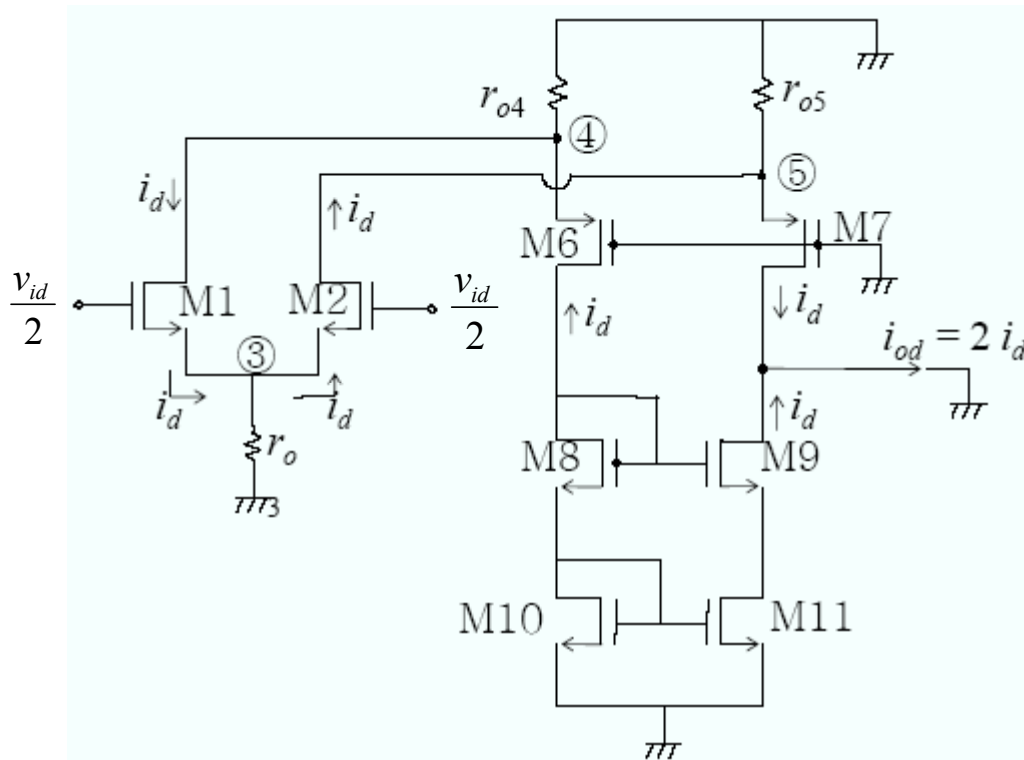


$$i_d = \frac{v_{id}}{r_{s1} + r_{s2}} = \frac{1}{2} g_{m1} v_{id}$$

$$G_{md} = \frac{i_{od}}{v_{id}} = \frac{2i_d}{v_{id}} = g_{m1}$$

(cont'd) Single Ended Folded Cascode Op Amp

- Rout

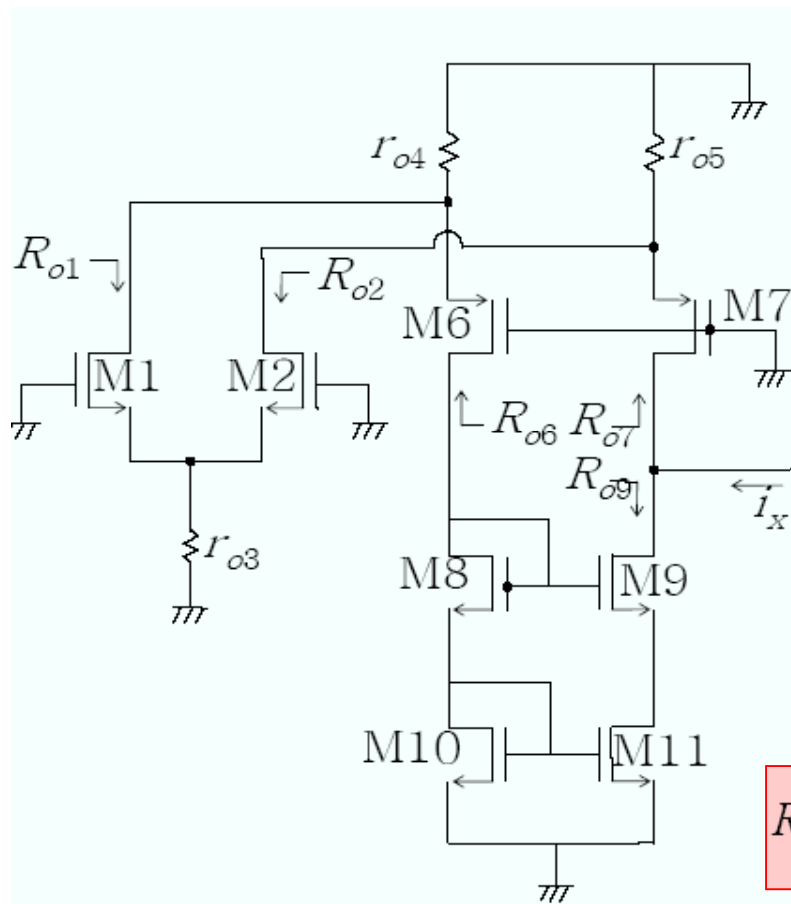

$$R_{o1} = g_{m1}r_{o1} \cdot (r_{s2} \parallel r_{o3}) + r_{o1} + (r_{s2} \parallel r_{o3}) \approx 2r_{o1}$$

$$R_{o6} = g_{m6}r_{o6} \cdot (R_{o1} \parallel r_{o4}) + r_{o6} + (R_{o1} \parallel r_{o4}) \approx g_{m6}r_{o6} \cdot (R_{o1} \parallel r_{o4})$$

$$R_{o7} = g_{m7} r_{o7} \cdot ((2r_{o2}) \parallel r_{o5}) = R_{o6}$$

$$R_{o9} = g_{m9}r_{o9} \cdot r_{o11} + r_{o9} + r_{o11} \approx g_{m9}r_{o9} \cdot r_{o11}$$

$$i_x = i_{x7} + i_{x9}$$

$$i_{x7} = \frac{v_x}{R_{o7}} \cdot \left(1 + \frac{r_{o5}}{r_{o5} + R_{o2}} \right) \approx \frac{v_x}{(g_{m7} r_{o7}) \cdot (r_{o2} \parallel r_{o5})}$$

$$i_{x9} = \frac{v_x}{R_{o9}}$$

$$R_o = \frac{v_x}{i_x} = \left\{ g_{m7} r_{o7} \cdot (r_{o2} \parallel r_{o5}) \right\} \parallel \left\{ g_{m9} r_{o9} \cdot r_{o11} \right\}$$

(cont'd) Single Ended Folded Cascode Op Amp

■ Design Process (1/3)

➤ Model Parameter Extraction

- k_n : 55.84 $\mu\text{A}/\text{V}^2$
- k_p : 23.51 $\mu\text{A}/\text{V}^2$
- λ_n : 0.025
- λ_p : 0.055
- V_{thn} : 0.776 V
- V_{thp} : 0.858 V

➤ Assign Current from Power Consumption Spec.

- Total Current : 0.375 mA
- Input pair : 0.125 mA
- Current mirror : 0.25 mA

(cont'd) Single Ended Folded Cascode Op Amp

■ Design Process (2/3)

- Determine W3 from CM_min, CM_max Spec.

- CM_min

$$V_{SS} + V_{DSAT3} + V_{GS1} = V_{SS} + V_{DSAT3} + V_{DSAT1} + V_{THn1}$$

- CM_max

$$V_{DD} - |V_{DSAT4}| + V_{THn1}$$

- Determine W4~W7 and Bias2 from Vout_max Spec.

- Vout_max : $V_{B2} + |V_{THp7}|$ → Determine VB2

- Assign Vdsat of M4,5 and M6,7 from Vout_max Spec

- Eg) Vout_max=4V → Vdsat of M4,5= 0.6V, Vdsat of M6,7 = 0.4V

- Calculate W4~7 to satisfy Vdsat & Ids of M4~7

- Determine W8~W11 from Vout_min Spec.

- Assign Vdsat of M8~M11 from Vout_min Spec.

- Eg) Vout_min=0.8V → Vdsat of M8~11 = 0.4V

- Calculate W8~11 to satisfy Vdsat and Ids of M8~11

(cont'd) Single Ended Folded Cascode Op Amp

■ Design Process (3/3)

➤ Determine W1,2 from Gain Spec.

- Calculate Rout_tot

$$R_o = \frac{v_x}{i_x} = \left\{ g_{m7}r_{o7} \cdot (r_{o2} \parallel r_{o5}) \right\} \parallel \left\{ g_{m9}r_{o9} \cdot r_{o11} \right\}$$

- Calculate Required Gm value to satisfy Gain Spec.

- Gain = Gm*Rout


- Calculate W1,2 from Gm

➤ Check other Spec. and Repeat the design process to optimize transistors size

- Slew Rate
- CM_min Check required
- CMRR, PSRR
- Check and Modify Bias Voltage to optimize transistor size.

(cont'd) Single Ended Folded Cascode Op Amp


■ Frequency Analysis

 

$$A_{vd} = g_{m1} R_o \quad |p_1| = \frac{1}{R_o C_L} \quad \omega_T = \frac{g_{m1}}{C_L} \quad |p_2| = \frac{1}{r_{s6} C_6}$$

(cont'd) Single Ended Folded Cascode Op Amp


■ Design Example

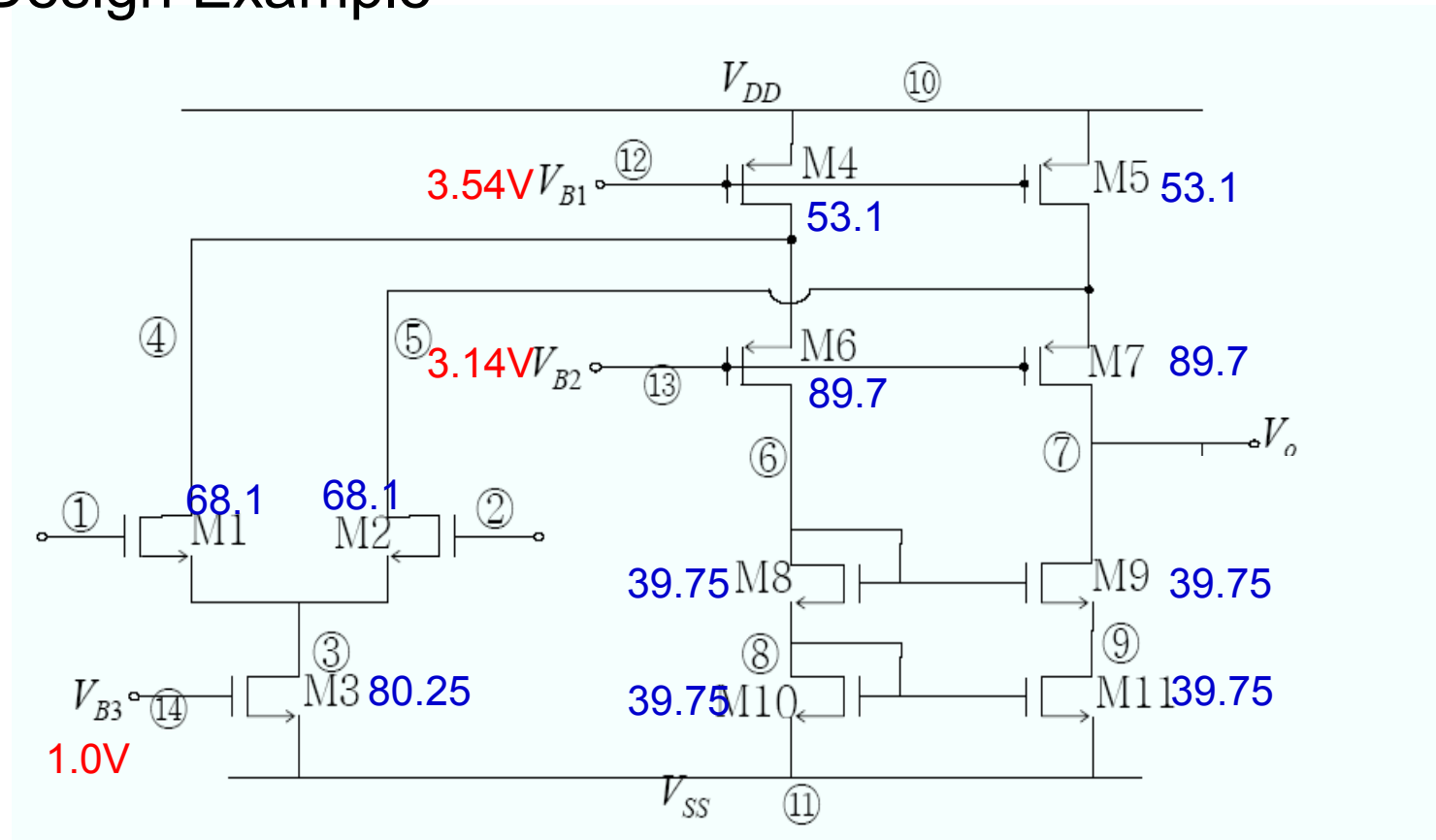

Calculated Gain= 3000 (70dB)

(cont'd) Single Ended Folded Cascode Op Amp

■ Simulation Result

 

Gain: **68dB**

BW: 170MHz

Loading: 2pF

Folded Cascode Op Amp with CMFB

Slew Rate Enhanced Folded Cascode Op Amp

References

- Joongho Choi, “CMOS analog IC Design,” IDEC Lecture Note, Mar. 1999.
- B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2001.
- Hongjun Park, “CMOS Analog Integrated Circuits Design,” Sigma Press, 1999.